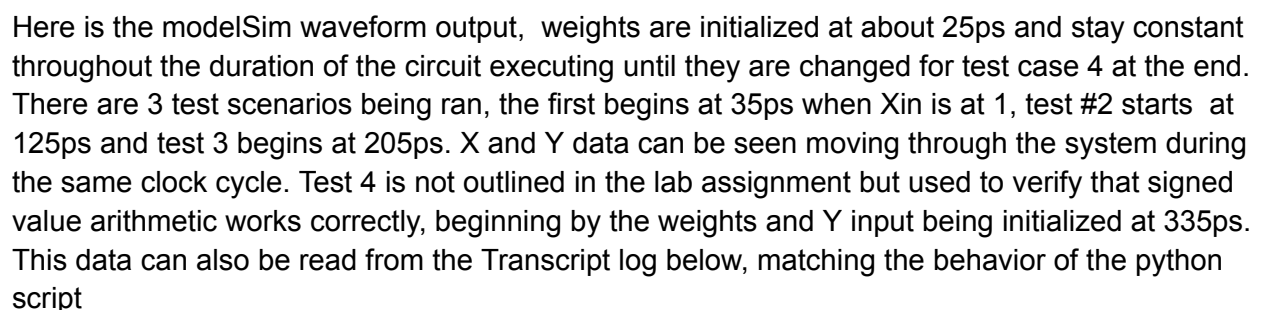


Clock Control Discussion: Consider and explain how the X and Y flip-flops should be controlled by the clock. Briefly describe any important considerations to ensure the slice operates correctly (e.g., proper edge sensitivity, timing of value transfers, or avoiding race conditions).

ModelSim Output:



```
# Systolic Array Testbench
# INPUT_WIDTH=8, ACCUM_WIDTH=32
# [35] INIT | W=[2,3,4] X in=0 Yprev=0 | Y0=0 Y1=0 Y2=x
```

```

# [45] X=1 | W=[2,3,4] X_in=1 Yprev=0 | Y0=0 Y1=0 Y2=0
# [55] X=2 | W=[2,3,4] X_in=2 Yprev=0 | Y0=0 Y1=0 Y2=0
# [65] X=3 | W=[2,3,4] X_in=3 Yprev=0 | Y0=2 Y1=0 Y2=0
# [75] X=4 | W=[2,3,4] X_in=4 Yprev=0 | Y0=4 Y1=5 Y2=0
# [85] PROP | W=[2,3,4] X_in=0 Yprev=0 | Y0=6 Y1=10 Y2=9
# [95] PROP | W=[2,3,4] X_in=0 Yprev=0 | Y0=8 Y1=15 Y2=18
# [105] PROP | W=[2,3,4] X_in=0 Yprev=0 | Y0=0 Y1=20 Y2=27
# [115] PROP | W=[2,3,4] X_in=0 Yprev=0 | Y0=0 Y1=0 Y2=36
# [125] PROP | W=[2,3,4] X_in=0 Yprev=0 | Y0=0 Y1=0 Y2=0
# [135] INIT | W=[2,3,4] X_in=0 Yprev=100 | Y0=0 Y1=0 Y2=0
# [145] X=5 | W=[2,3,4] X_in=5 Yprev=100 | Y0=100 Y1=0 Y2=0
# [155] X=10 | W=[2,3,4] X_in=10 Yprev=100 | Y0=100 Y1=100 Y2=0
# [165] PROP | W=[2,3,4] X_in=0 Yprev=100 | Y0=110 Y1=100 Y2=100
# [175] PROP | W=[2,3,4] X_in=0 Yprev=100 | Y0=120 Y1=125 Y2=100
# [185] PROP | W=[2,3,4] X_in=0 Yprev=100 | Y0=100 Y1=150 Y2=145
# [195] PROP | W=[2,3,4] X_in=0 Yprev=100 | Y0=100 Y1=100 Y2=190
# [205] PROP | W=[2,3,4] X_in=0 Yprev=100 | Y0=100 Y1=100 Y2=100
# [215] INIT | W=[2,3,4] X_in=0 Yprev=0 | Y0=100 Y1=100 Y2=100
# [225] S1:1 | W=[2,3,4] X_in=1 Yprev=0 | Y0=0 Y1=100 Y2=100
# [235] S2:10 | W=[2,3,4] X_in=10 Yprev=0 | Y0=0 Y1=0 Y2=100
# [245] S1:2 | W=[2,3,4] X_in=2 Yprev=0 | Y0=2 Y1=0 Y2=0
# [255] S2:20 | W=[2,3,4] X_in=20 Yprev=0 | Y0=20 Y1=5 Y2=0
# [265] S1:3 | W=[2,3,4] X_in=3 Yprev=0 | Y0=4 Y1=50 Y2=9
# [275] S2:30 | W=[2,3,4] X_in=30 Yprev=0 | Y0=40 Y1=10 Y2=90
# [285] PROP | W=[2,3,4] X_in=0 Yprev=0 | Y0=6 Y1=100 Y2=18
# [295] PROP | W=[2,3,4] X_in=0 Yprev=0 | Y0=60 Y1=15 Y2=180
# [305] PROP | W=[2,3,4] X_in=0 Yprev=0 | Y0=0 Y1=150 Y2=27
# [315] PROP | W=[2,3,4] X_in=0 Yprev=0 | Y0=0 Y1=0 Y2=270
# [325] PROP | W=[2,3,4] X_in=0 Yprev=0 | Y0=0 Y1=0 Y2=0
# [335] PROP | W=[2,3,4] X_in=0 Yprev=0 | Y0=0 Y1=0 Y2=0
# [345] INIT | W=[-2,3,-1] X_in=0 Yprev=-10 | Y0=0 Y1=0 Y2=0
# [355] X=-5 | W=[-2,3,-1] X_in=-5 Yprev=-10 | Y0=-10 Y1=0 Y2=0
# [365] X=4 | W=[-2,3,-1] X_in=4 Yprev=-10 | Y0=-10 Y1=-10 Y2=0
# [375] PROP | W=[-2,3,-1] X_in=0 Yprev=-10 | Y0=0 Y1=-10 Y2=-10
# [385] PROP | W=[-2,3,-1] X_in=0 Yprev=-10 | Y0=-18 Y1=-15 Y2=-10
# [395] PROP | W=[-2,3,-1] X_in=0 Yprev=-10 | Y0=-10 Y1=-6 Y2=-10
# [405] PROP | W=[-2,3,-1] X_in=0 Yprev=-10 | Y0=-10 Y1=-10 Y2=-10
# [415] PROP | W=[-2,3,-1] X_in=0 Yprev=-10 | Y0=-10 Y1=-10 Y2=-10
# All test cases completed

```

Python Output:

Systolic Array Python Simulation

INPUT_WIDTH=8, ACCUM_WIDTH=32

EST CASE 1: Yprev = 0

| | |
|------|---|
| INIT | W=[2, 3, 4] X_in= 0 Yprev= 0 Y0= 0 Y1= 0 Y2= 0 |
| X=1 | W=[2, 3, 4] X_in= 1 Yprev= 0 Y0= 0 Y1= 0 Y2= 0 |
| X=2 | W=[2, 3, 4] X_in= 2 Yprev= 0 Y0= 0 Y1= 0 Y2= 0 |
| X=3 | W=[2, 3, 4] X_in= 3 Yprev= 0 Y0= 2 Y1= 0 Y2= 0 |
| X=4 | W=[2, 3, 4] X_in= 4 Yprev= 0 Y0= 4 Y1= 5 Y2= 0 |
| PROP | W=[2, 3, 4] X_in= 0 Yprev= 0 Y0= 6 Y1= 10 Y2= 9 |
| PROP | W=[2, 3, 4] X_in= 0 Yprev= 0 Y0= 8 Y1= 15 Y2= 18 |
| PROP | W=[2, 3, 4] X_in= 0 Yprev= 0 Y0= 0 Y1= 20 Y2= 27 |
| PROP | W=[2, 3, 4] X_in= 0 Yprev= 0 Y0= 0 Y1= 0 Y2= 36 |
| PROP | W=[2, 3, 4] X_in= 0 Yprev= 0 Y0= 0 Y1= 0 Y2= 0 |

TEST CASE 2: Non-zero Yprev

| | |
|------|---|
| INIT | W=[2, 3, 4] X_in= 0 Yprev= 100 Y0= 0 Y1= 0 Y2= 0 |
| X=5 | W=[2, 3, 4] X_in= 5 Yprev= 100 Y0= 100 Y1= 0 Y2= 0 |
| X=10 | W=[2, 3, 4] X_in= 10 Yprev= 100 Y0= 100 Y1= 100 Y2= 0 |
| PROP | W=[2, 3, 4] X_in= 0 Yprev= 100 Y0= 110 Y1= 100 Y2= 100 |
| PROP | W=[2, 3, 4] X_in= 0 Yprev= 100 Y0= 120 Y1= 125 Y2= 100 |
| PROP | W=[2, 3, 4] X_in= 0 Yprev= 100 Y0= 100 Y1= 150 Y2= 145 |
| PROP | W=[2, 3, 4] X_in= 0 Yprev= 100 Y0= 100 Y1= 100 Y2= 190 |
| PROP | W=[2, 3, 4] X_in= 0 Yprev= 100 Y0= 100 Y1= 100 Y2= 100 |

TEST CASE 3: Interleaved Streams

| | |
|-------|---|
| INIT | W=[2, 3, 4] X_in= 0 Yprev= 0 Y0= 100 Y1= 100 Y2= 100 |
| S1:1 | W=[2, 3, 4] X_in= 1 Yprev= 0 Y0= 0 Y1= 100 Y2= 100 |
| S2:10 | W=[2, 3, 4] X_in= 10 Yprev= 0 Y0= 0 Y1= 0 Y2= 100 |
| S1:2 | W=[2, 3, 4] X_in= 2 Yprev= 0 Y0= 2 Y1= 0 Y2= 0 |
| S2:20 | W=[2, 3, 4] X_in= 20 Yprev= 0 Y0= 20 Y1= 5 Y2= 0 |
| S1:3 | W=[2, 3, 4] X_in= 3 Yprev= 0 Y0= 4 Y1= 50 Y2= 9 |
| S2:30 | W=[2, 3, 4] X_in= 30 Yprev= 0 Y0= 40 Y1= 10 Y2= 90 |
| PROP | W=[2, 3, 4] X_in= 0 Yprev= 0 Y0= 6 Y1= 100 Y2= 18 |
| PROP | W=[2, 3, 4] X_in= 0 Yprev= 0 Y0= 60 Y1= 15 Y2= 180 |
| PROP | W=[2, 3, 4] X_in= 0 Yprev= 0 Y0= 0 Y1= 150 Y2= 27 |
| PROP | W=[2, 3, 4] X_in= 0 Yprev= 0 Y0= 0 Y1= 0 Y2= 270 |
| PROP | W=[2, 3, 4] X_in= 0 Yprev= 0 Y0= 0 Y1= 0 Y2= 0 |
| PROP | W=[2, 3, 4] X_in= 0 Yprev= 0 Y0= 0 Y1= 0 Y2= 0 |

TEST CASE 4: Negative Arithmetic Validation

INIT | W=[-2, 3,-1] X_in= 0 Yprev= -10 | Y0= 0 Y1= 0 Y2= 0
X=-5 | W=[-2, 3,-1] X_in= -5 Yprev= -10 | Y0= -10 Y1= 0 Y2= 0
X=4 | W=[-2, 3,-1] X_in= 4 Yprev= -10 | Y0= -10 Y1= -10 Y2= 0
PROP | W=[-2, 3,-1] X_in= 0 Yprev= -10 | Y0= 0 Y1= -10 Y2= -10
PROP | W=[-2, 3,-1] X_in= 0 Yprev= -10 | Y0= -18 Y1= -15 Y2= -10
PROP | W=[-2, 3,-1] X_in= 0 Yprev= -10 | Y0= -10 Y1= -6 Y2= -10
PROP | W=[-2, 3,-1] X_in= 0 Yprev= -10 | Y0= -10 Y1= -10 Y2= -10
PROP | W=[-2, 3,-1] X_in= 0 Yprev= -10 | Y0= -10 Y1= -10 Y2= -10
All test cases completed